

(4)

Code No. : B-225(B)

Roll No.....

ZalĀa-2. Draw the circuit diagram of fixed bias circuit and derive the expression for the stability factors.

Draw the circuit diagram of fixed bias circuit and derive the expression for the stability factors.

OR

Explain the characteristic curve of a PNP transistor in common base (CB) mode.

Explain the characteristic curve of a PNP transistor in common base (CB) mode.

ZalĀa-3. Explain the working of a RC coupled amplifier with circuit diagram and write its advantages.

Explain the working of a RC coupled amplifier with circuit diagram and write its advantages.

OR

Derive an expression for voltage gain of negative voltage feedback amplifier with circuit diagram.

Derive an expression for voltage gain of negative voltage feedback amplifier with circuit diagram.

ZalĀa-4. Explain the working of a cascading (double) tuned amplifier with circuit diagram.

Explain the working of a cascading (double) tuned amplifier with circuit diagram.

OR

Explain tuned class 'C' amplifier with diagram.

Explain tuned class 'C' amplifier with diagram.

ZalĀa-5. How is an OP-AMP used as non inverting amplifier? Explain.

How is an OP-AMP used as non inverting amplifier? Explain.

OR

What are Adder and Subtractor? Explain.

What are Adder and Subtractor? Explain.

Code No. : B-225(B)

Annual Examination - 2017

B.Sc.-I

ELECTRONICS

Paper - II

LINEAR ACTIVE CIRCUITS

Max.Marks : 50

Min Marks : 17

Time : 3 Hrs.

Note: Section 'A' , containing 10 very short answer type questions, is compulsory. Section 'B' consists of short answer type questions and Section 'C' consists of long answer type questions. Section 'A' has to be solved first.

Note: Section 'A' , containing 10 very short answer type questions, is compulsory. Section 'B' consists of short answer type questions and Section 'C' consists of long answer type questions. Section 'A' has to be solved first.

(Section-'A')

(Answer the following very short-answer-type questions in one or two sentences) (1x10=10)

ZalĀa-1. What do you understand by diode?

What do you understand by diode?

ZalĀa-2. What is meant by 'Depletion Layer'?

What is meant by 'Depletion Layer'?

ZalĀa-3. What is the function of transistor?

What is the function of transistor?

ZalĀa-4. What is the function of base in a transistor?

What is the function of base in a transistor?

ZalĀa-5. Write the advantages of negative voltage feedback amplifier.

Write the advantages of negative voltage feedback amplifier.

ZalĀa-6. Write the utility of h parameters.

Write the utility of h parameters.

(2)

Code No. : B-225(B)

ZalĀa-7. Zavoŷy āŷyçŷyĴmçĴĴē?

What are amplifiers?

ZalĀa-8. 1ĴĀĀpZavoŷy ŷĵa ŷyçēŷŷy Equāā rmatŷ ĴĴ

Write any one use of tuned amplifier.

ZalĀa-9. āŷyā ĀāvŌa ŷŷy āvŷ ; āvĴuŷy Zāmrb ŷŷy āā Ŵē?

What is the required condition for an oscillator?

ZalĀa-10. wāā ārk ĀāvŌa ŷŷy ; āvāā qēāy ŷŷy āā Ŵē?

What is the range of frequency for Wein Bridge oscillator?

hĴĴ-r' (Section-'B')

āāāāāŷyĴm vi ā ēĴēāu ZalĀāp ŷŷy ēĴē 150-200 Ŵāā-yāā tĴĴ ĀĴĴ

(Answer the following short-answer type questions with word limit 150-200) (3x5=15)

ZalĀa-1. ŷŷy ; oēĴā āā ŷŷyā ŷŷy āŷyāāāō qāēqn rāŷŷē ytl āŷŷ ĴĴ

Explain the working of a half wave rectifier with a neat diagram.

OR

kāē »ĴāāpŷyçwāĴĴ ēĴāāçĴē ŷŷy sāā Equāā tĴŷŷyçvāā kāā Ŵē qāēqn rāŷŷē ytl āŷŷ ĴĴ

How can a zener diode be used as voltage regulator? Explain with circuit diagram.

ZalĀa-2. ēŷuāāĴŷyĴāāāōā tĴĴĴĴĴē ŷŷy ēŷyçŷyōāā 6mA mnā ; āāē oāā

Ŵēñ mnā ŷŷy tāā Ōāā ŷŷyĴāçŷŷy ĴĴ

In common collector mode of a transistor, emitter current is _____ and base current is _____. Find the value of _____ and _____.

OR

1ĴĴĴĴĴē ŷŷy rāūāŷyā yç ; āq ŷŷy āā ytl mçĴē? wāĴĴĴ āvsāçŷŷy rāūāŷyā āvāō ŷŷyç ytl āŷŷ ĴĴ

What do you understand by transistor biasing? Describe the voltage divider biasing method.

ZalĀa-3. 1ĴĴĴĴĴē ŷŷy _____ mnā āvāō tĴ qēātāĴē ŷŷy āvŷ ytmāu qāēqn rāççuçĴĴ

Draw the equivalent circuit for h parameters in _____ and _____ mode of a transistor.

(3)

Code No. : B-225(B)

OR

ŷŷy ; Ĵq āŷāāv Zavoŷy ŷĵa qāēqn rāŷŷē wāĴĴĴ vās, oāā vās ŷŷy āvŷ Ĵūçŷŷy ZalĴm ŷŷyĴāçŷŷy ĴĴ

Draw a circuit diagram of small signal amplifier and derive an expression for voltage gain and current gain.

ZalĀa-4. ŷŷyĴv 1ĴĴĴĴĴē ŷŷy āā Ŵē çyŷŷā ytmāu qāēqn tĴāvĴçĴā ŷŷyĴāçŷŷy ĴĴ

What is single tuned amplifier? Analyse it, in A.C. equivalent circuit.

OR

1ĴĴĴĴĴē ŷŷyçwāĴĴ Ąu ZavoŷyçtĴē ; mē āvāŷŷy mnā 1ĴĴĴĴĴē çŷŷy vāsçŷŷy wĴāā ŷŷyĴāçŷŷy ĴĴ

Differentiate tuned amplifiers from other amplifiers and write the advantages of tuned amplifier.

ZalĀa-5. wāā ārk ĀāvŌa qāēqn rāŷŷē çyŷŷy ŷŷyāāāō ytl āŷŷ ĴĴ

Explain the working of Wein bridge oscillator with diagram.

OR

ŴāĴçZavoŷy ŷĵa qāēqn rāŷŷē çyŷŷy ŷŷyāāāō āvāŷŷy ĴĴ

Explain the working of Hartley oscillator with diagram.

hĴĴ-y' (Section-'C')

āāāāāŷyĴm Āāi ē ēĴēāu ZalĀāp ŷŷy ēĴē 300-350 Ŵāā-yāā tĴĴ ĀĴĴ

(Answer the following long-answer type questions with word limit 300-350) (5x5=25)

ZalĀa-1. āŷŷĴē ŷŷy āā ŷŷyā ŷŷy āāāāāō wāĴĴĴ yç yç Ŵāā āŷŷĴē āŷŷy Zāŷŷē çŷŷy ŷŷy ŷŷyēā Ŵē?

What is a filter? How does _____ section filter reduce the ripple factor in the output of a rectifier?

OR

PN kĴŴāā »Ĵāāpŷŷy ; āsvāāāŷŷy wŷŷy qāēqn rāŷŷē ytl āŷŷ mnā Ŵnāmŷŷy wāāmŷŷy Zāmēāç ŷŷy āvŷ Ĵūçŷŷy āvāŷŷy ĴĴ

Explain the characteristic curve of a PN junction diode with circuit diagram and write the expression for static and dynamic resistance.